

## EXPERIMENT-1

12/09/2011

# Ohm's Law

AIM:- To find the resistance per unit length of a given wire by plotting a graph of potential difference versus current.

### APPARATUS REQUIRED:-

The unknown resistor, ammeter, voltmeter, rheostat, battery, key and connecting wire.

CIRCUIT DIAGRAM:- (see alongside)

### THEORY AND FORMULA:-

Ohm's law states that current flowing through a conductor is directly proportional to the potential difference across its ends provided the physical conditions remain the same i.e.  $V \propto I$

### PROCEDURE:-

- 1) Make correct connections using the connecting wire by referring the circuit diagram.
- 2) Voltmeter records the potential difference across

the unknown resistance 'R' and ammeter records the current flowing through unknown resistance 'R'.

- 3) A rheostat  $R_h$  is connected in series with the cell as in the diagram.
- 4) Insert the key and adjust the rheostat so that a small current flows through the circuit.
- 5) Vary the current on the Rheostat and take five readings.
- 6) Plot the graph between  $V$  and  $I$ , taking  $V$  on the x-axis and  $I$  on the y-axis. It will be a straight line. The slope gives the unknown resistance.

**RESULT:-** The graph between  $V$  and  $I$  is a straight line.  
Resistance per unit length of the wire =  $0.66 \Omega/m$   
Resistance of the wire by calculation =  $4 \Omega$   
Resistance of the wire by the graph =  $4 \Omega$


### PRECAUTIONS:-

- 1) The connection must be neat and tight.
- 2) Always use low resistance rheostat.
- 3) Insert the plug in the key only while recording observations. Otherwise current flowing through the resistor will change its resistance.
- 4) ~~Zero error, if any, must be taken into account~~

## SOURCES OF ERROR:-

- 1) There may occur some contact resistance in the circuit.
- 2) The connecting wire may not have negligible resistance.
- 3) The unknown resistance of the metallic conductor may not be negligible when compared to that of the voltmeter.

~~Car & the~~

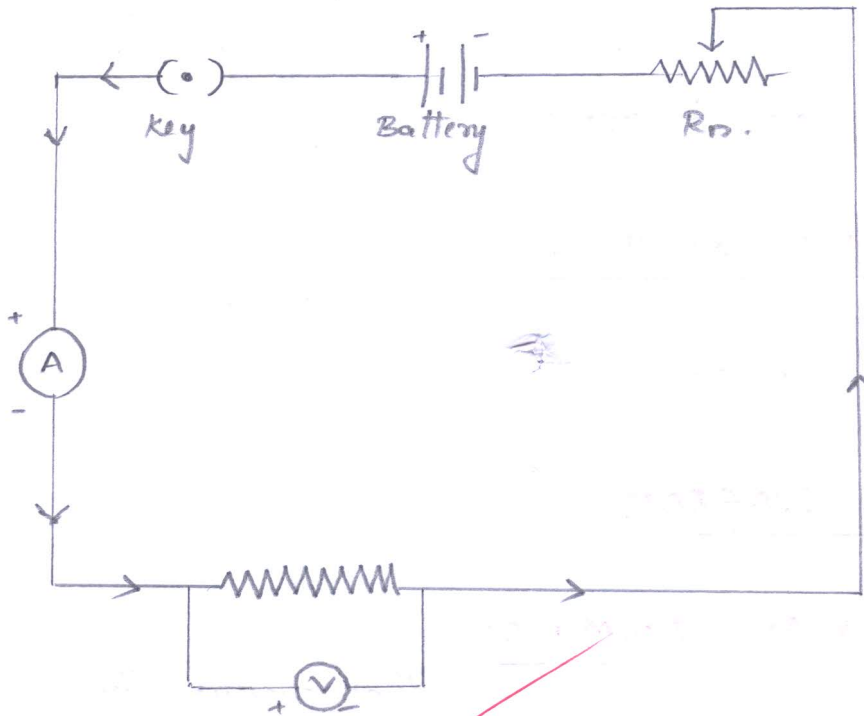

Least count of voltmeter = 0.02V  
 Least count of Ammeter = 0.01A

S No	Voltmeter reading (V)	Ammeter reading (A)	Resistance ( $R = V/I$ )
1	0.4	0.1	4 $\Omega$
2	0.8	0.2	4 $\Omega$
3	1.2	0.3	4 $\Omega$
4	1.6	0.4	4 $\Omega$
5	2.0	0.5	4 $\Omega$

mean resistance = 4  $\Omega$

length of the wire = 60cm

resistance per unit length = 6.66  $\Omega/m$

