
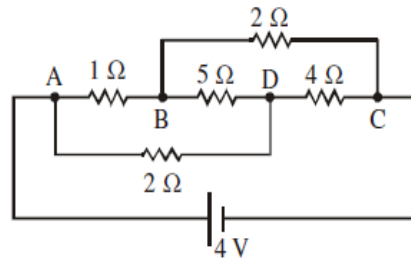


CURRENT ELECTRICITY

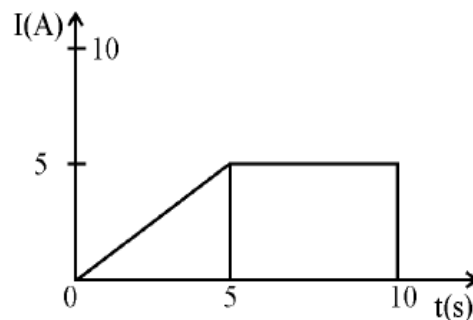- 1 Calculate the current drawn from the battery by the network of resistors shown in the figure.




- 2 (a) Deduce the relation between current I flowing through a conductor and drift velocity \vec{v}_d of the electrons.
 (b) Figure shows a plot of current ' I ' flowing through the cross-section of a wire versus the time ' t '. Use the plot to find the charge flowing in 10s through the wire.




- 3 Draw a circuit diagram of a potentiometer. State its working principle. Derive the necessary formula to describe how it is used to compare the emfs of the two cells.
 4 With the help of the circuit diagram, explain the working principle of meter bridge. How is it used to determine the unknown resistance of a given wire ? Write the necessary precautions to minimize the error in the result.
 5 Using the concept of drift velocity of charge carriers in a conductor, deduce the relationship between current density and resistivity of the conductor.

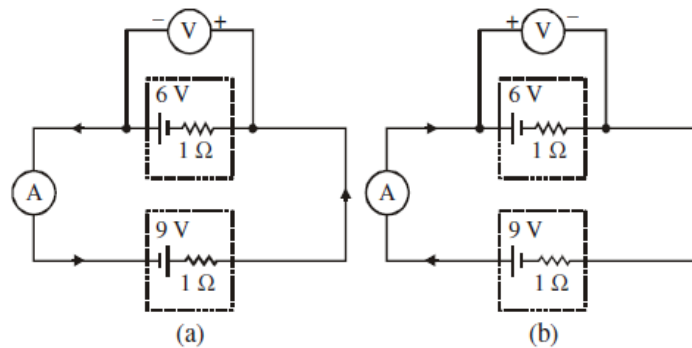- 6 In the two electric circuits shown in the figure, determine the readings of ideal ammeter (A) and the ideal voltmeter (V).



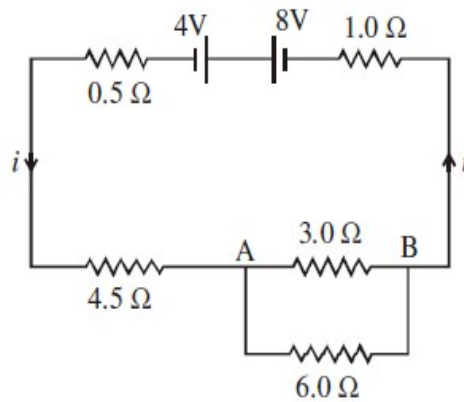- 7 In the circuit shown in the figure, find the current through each resistor.




- 8 A cell of emf 'E' and internal resistance 'r' is connected across a variable load resistor R. Draw the plots of the terminal voltage V versus (i) R and (ii) the current I.


It is found that when $R = 4 \Omega$, the current is 1 A and when R is increased to 9Ω , the current reduces to 0.5 A. Find the values of the emf E and internal resistance r.

- 9 Use Kirchhoff's rules to obtain conditions for the balance condition in a Wheatstone bridge.

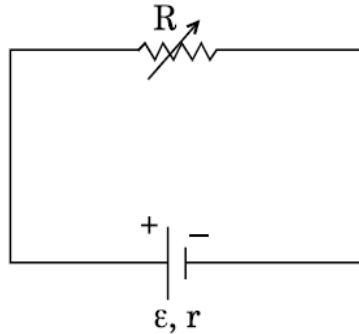
- 10 A variable resistor R is connected across a cell of emf ε and internal resistance r as shown in the figure. Draw a plot showing the variation of (i) terminal voltage V and (ii) the current I , as a function of R .




- 11 A potential difference V is applied across a conductor of length L and diameter D . How is the drift velocity, v_d , of charge carriers in the conductor affected when (i) V is halved, (ii) L is doubled and (iii) D is halved? Justify your answer in each case.
- 12 Two metallic resistors are connected first in series and then in parallel across a d.c. supply. Plot of $I - V$ graph is shown for the two cases. Which one represents a parallel combination of the resistors and why?

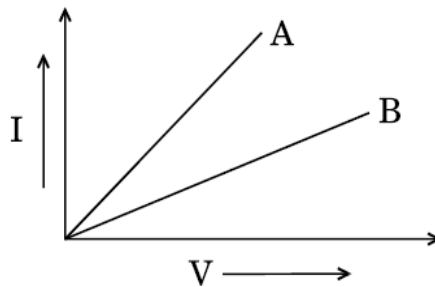

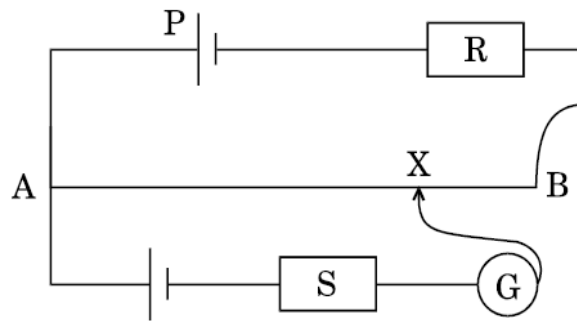- 13 In the potentiometer circuit shown, the null point is at X. State with reason, where the balance point will be shifted when
- resistance R is increased, keeping all other parameters unchanged;
 - resistance S is increased, keeping R constant.



- 14 Define the electric resistivity of a conductor.
 Plot a graph showing the variation of resistivity with temperature in the case of a (a) conductor, (b) semiconductor.
 Briefly explain, how the difference in the behaviour of the two can be explained in terms of number density of charge carriers and relaxation time.
- 15 Use Kirchhoff's rules to determine the potential difference between the points A and D when no current flows in the arm BE of the electric network shown in the figure.

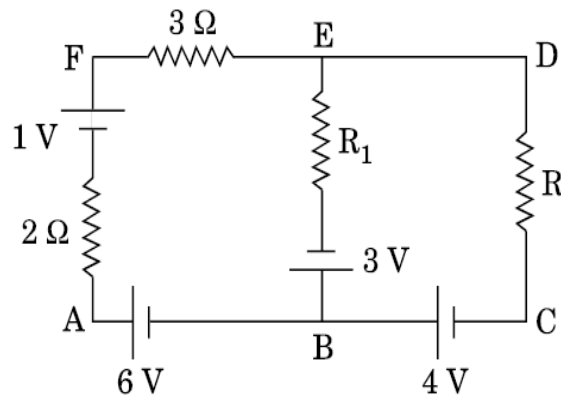

16 Find the relation between drift velocity and relaxation time of charge carriers in a conductor.

A conductor of length L is connected to a d.c. source of emf 'E'. If the length of the conductor is tripled by stretching it, keeping 'E' constant, explain how its drift velocity would be affected.